

Measuring Preamp Input Resistance in the Few to 50 Ω Range

Mitch Newcomer



October 6, 2014

Limits and Technique of the Measurement


Basic Idea -



- Create a step current using a resistor in series between a voltage pulser and the input of the preamp that is large compared to the expected preamp input resistance. The resistor should be very close to the amplifier input to avoid pickup. The input current is easy to calculate, easier to estimate as V step. (Measure dV caused by the current pulse at the input not the absolute V .)
- Use as large of a voltage step as feasible to avoid output saturation. I use 100mV across a 1K ohm resistor here. It could easily be 1V across 10K or even better 5V if the amplifier output isn't near saturation.
- Measure the signal at the input with a scope probe. The signal at the input will be fairly small, mV or smaller. So use the averaging on the scope with a 1mV scale if possible. The bandwidth will be somewhat limited so larger is better but still not likely to be more than 10mV while the output is in its linear range. The objective is to get $dV_{in}/I = Z_{in}$
- This method is fine for a 50 Ω input impedance and the technique can be proven by simply using it on a 50 Ω Resistor. Obviously if you can measure the input voltage on a 50 Ω resistor but it's too small to measure on the amplifier input, the Amp input is a lot smaller than 50 Ω which may be good enough.

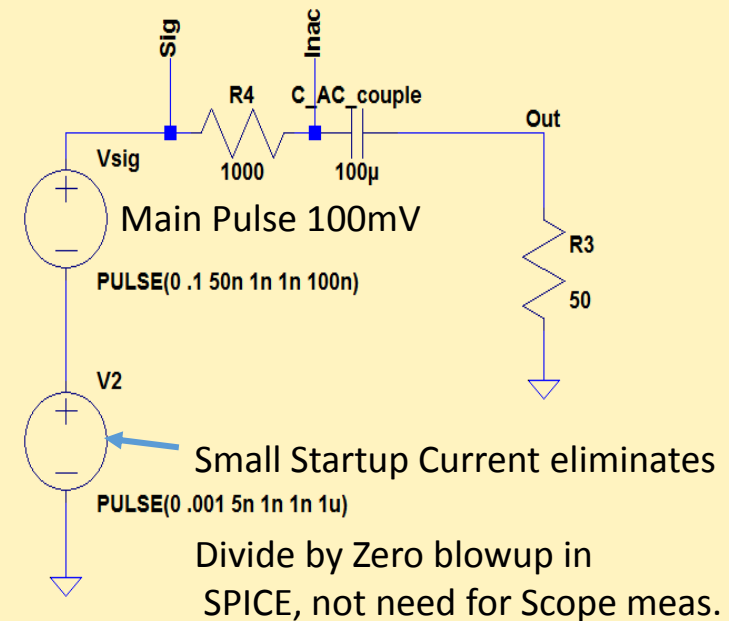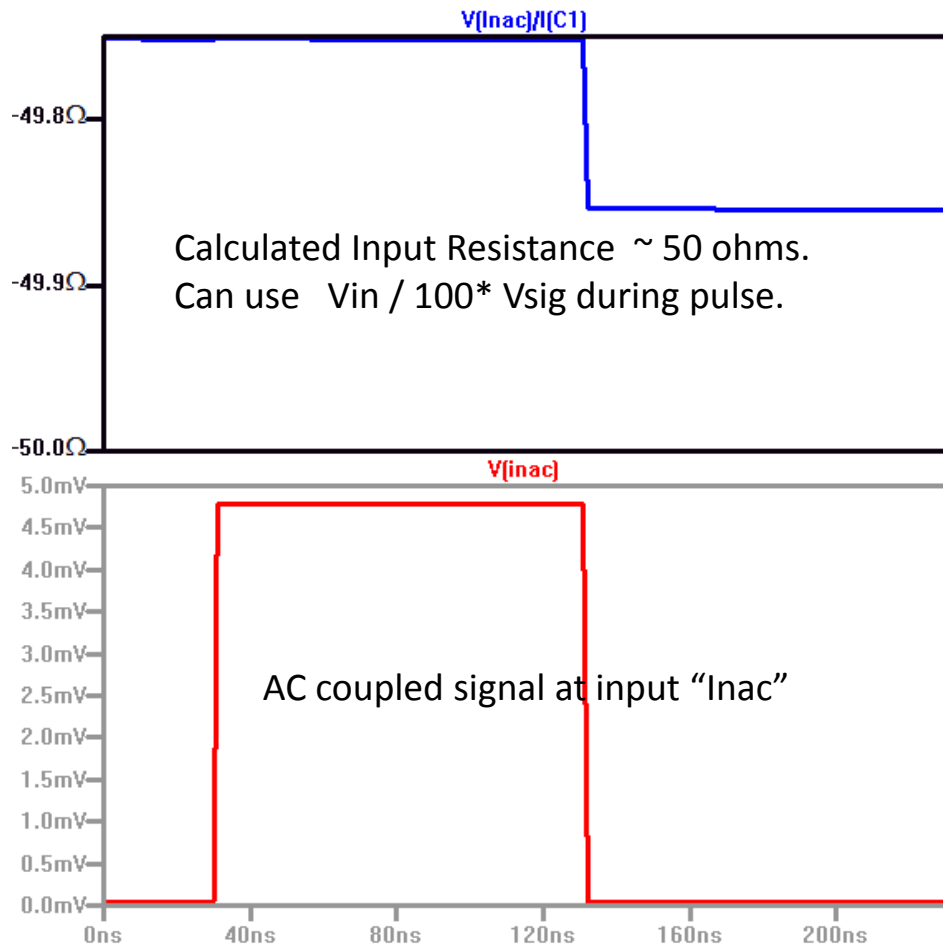Pulse Technique to measure a 50Ω Resistor




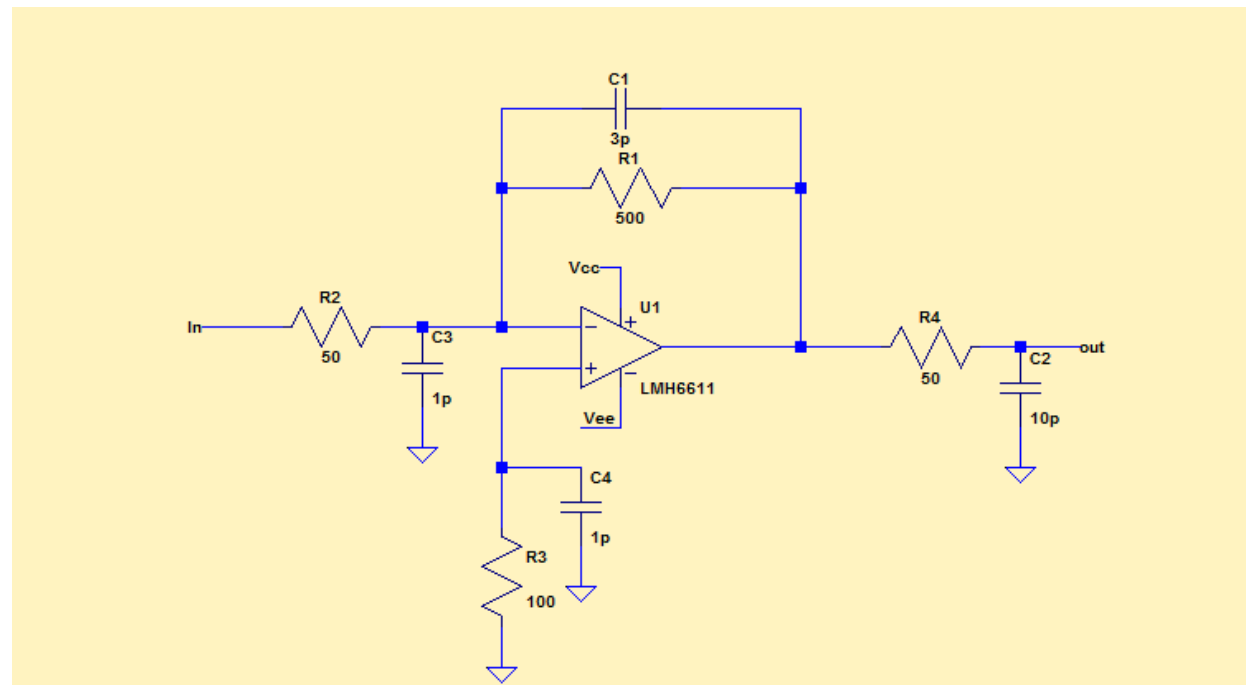400MHz LMH Op Amp Gain ~ 10 input 50Ω
to compare with 50Ω resistor.




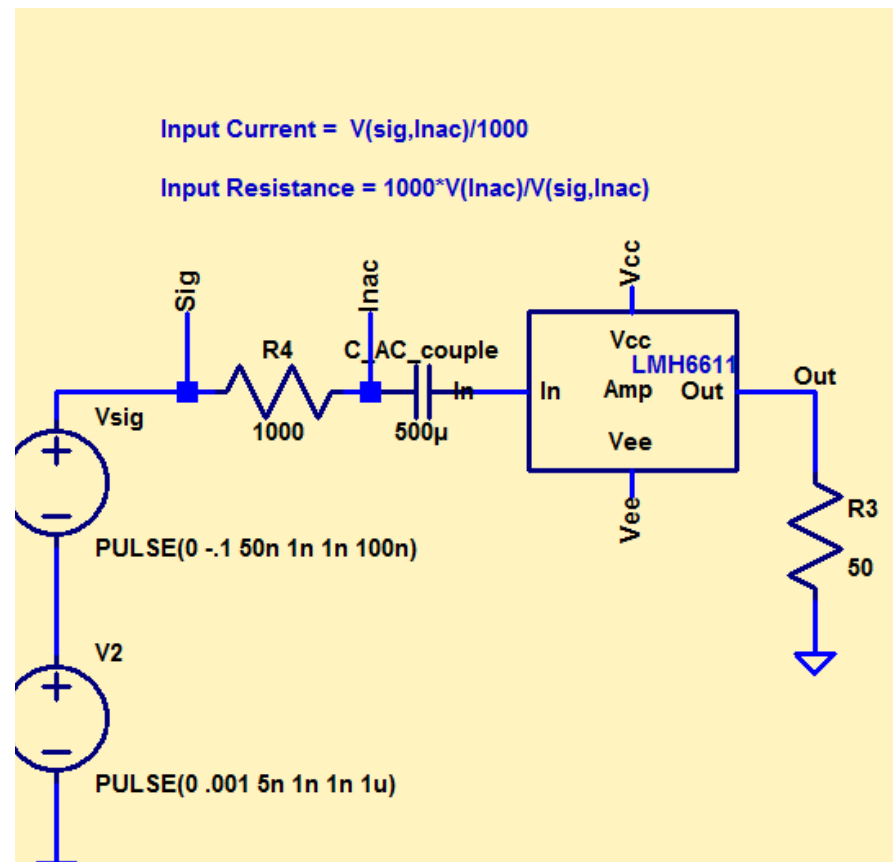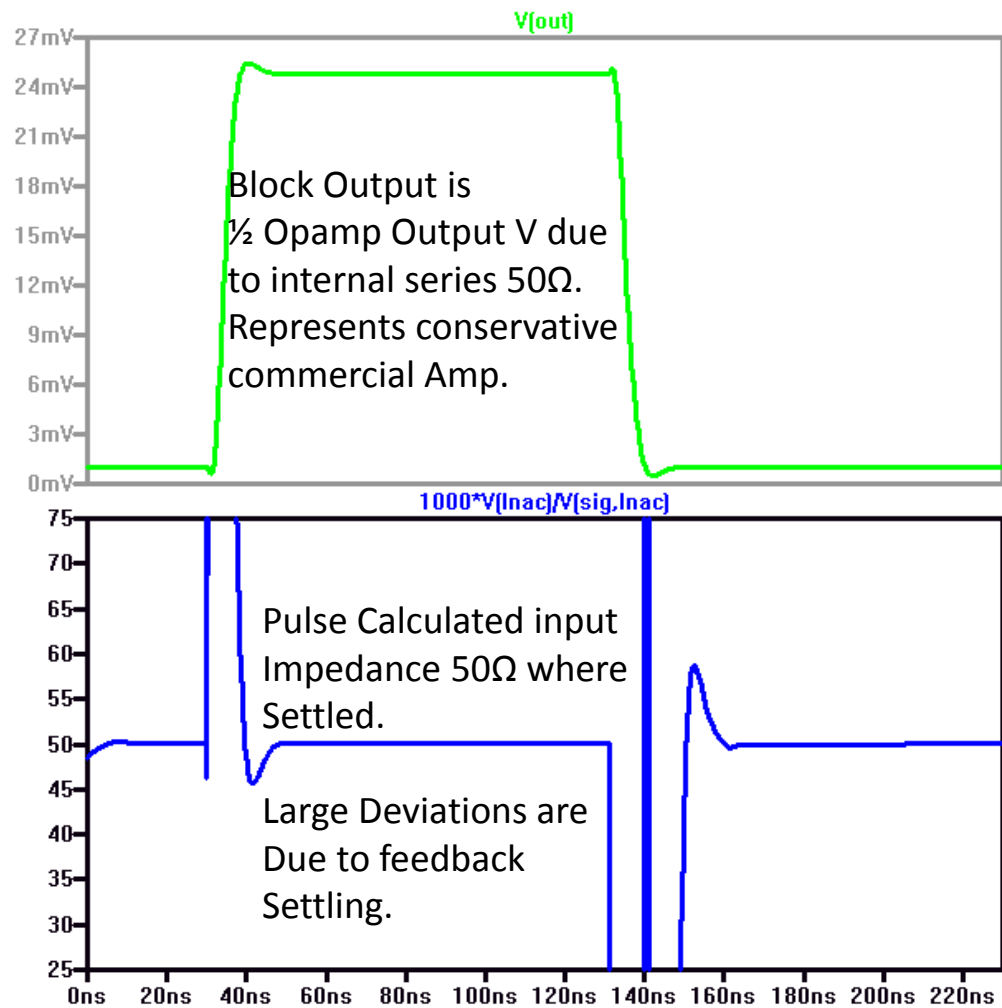



30pF Capacitance 50 Ω Resistor vs Opamp

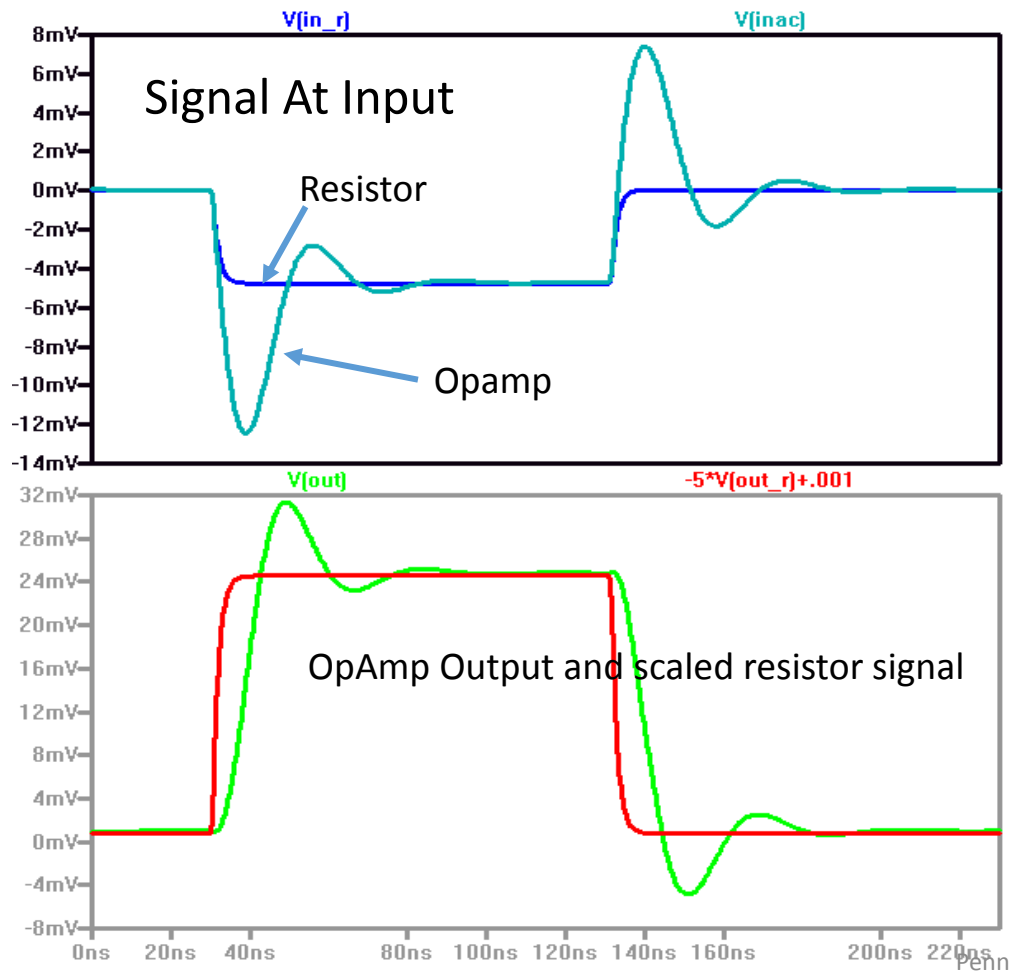

Add 30pF Capacitance

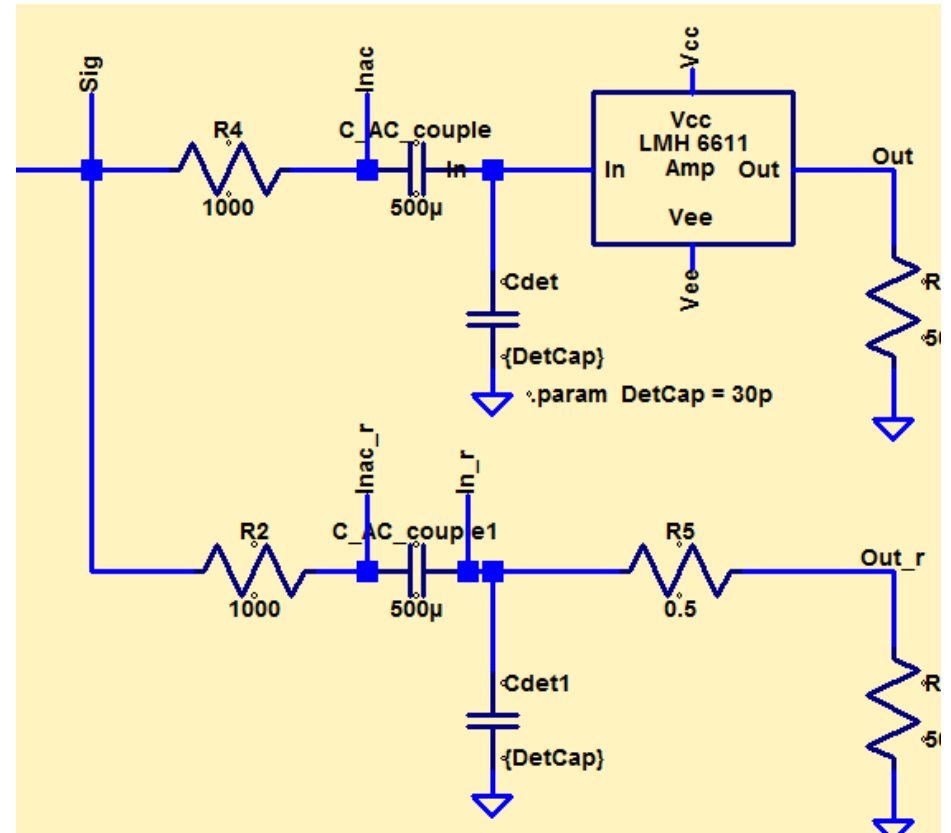

Fast Amp and 50Ω

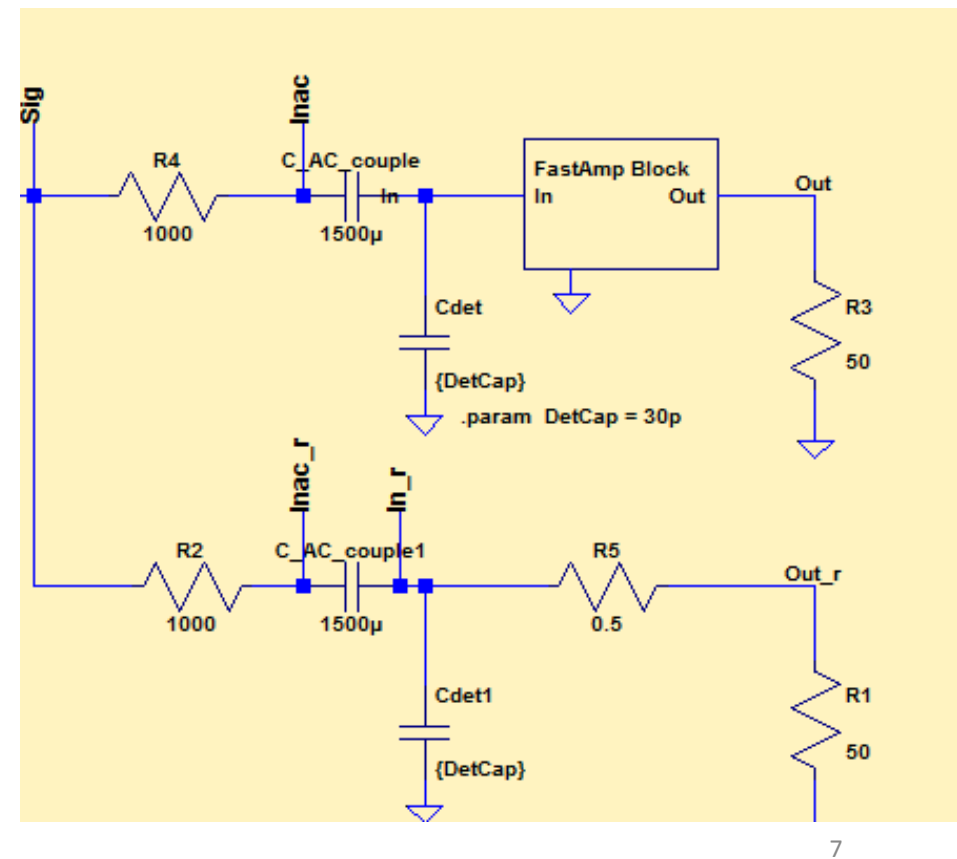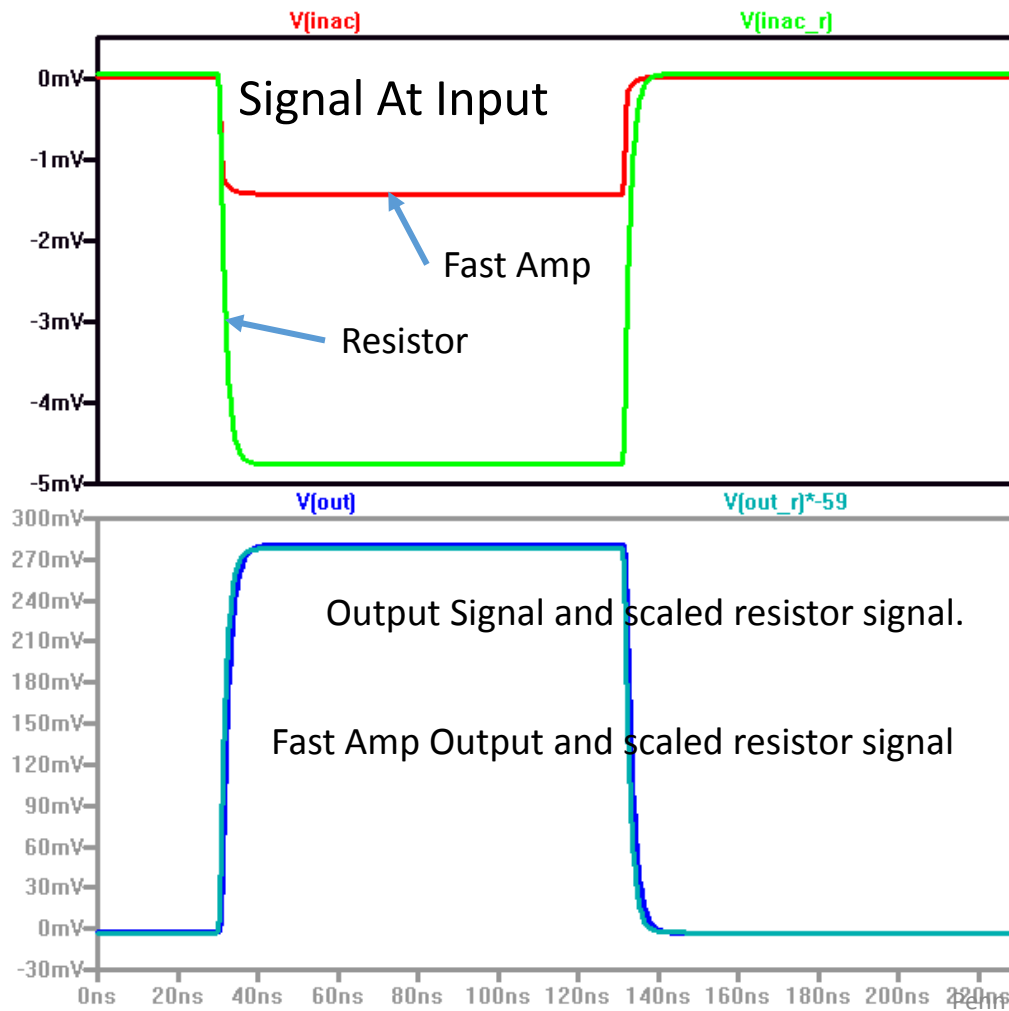

Pulse Calculated Input Resistance

