

## Preamp in voltage mode

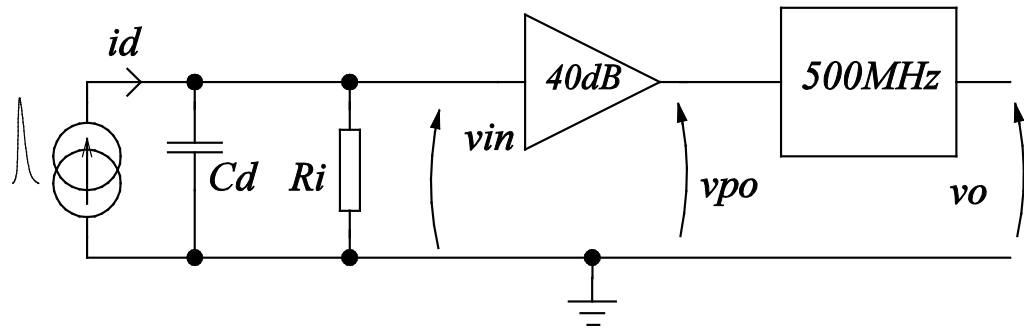


Fig1. Preamplifier working in voltage mode.


Response  $v_o(t)$  can be found solving following equations.

Voltages:

$$v_{in} = i_d \frac{1}{s C_d + \frac{1}{R_i}} = i_d \frac{R_i}{1 + s C_d R_i} \quad v_o = v_{in} K u(s) = v_{in} \frac{K u}{1 + s \tau_{p0}}$$

Where  $\tau_{p0}$  defines bandwidth of the amplifier (for 500MHz 3dB bandwidth  $\tau_{p0} = 0.32\text{ns}$ )

## Preamp in charge/transimpedance mode

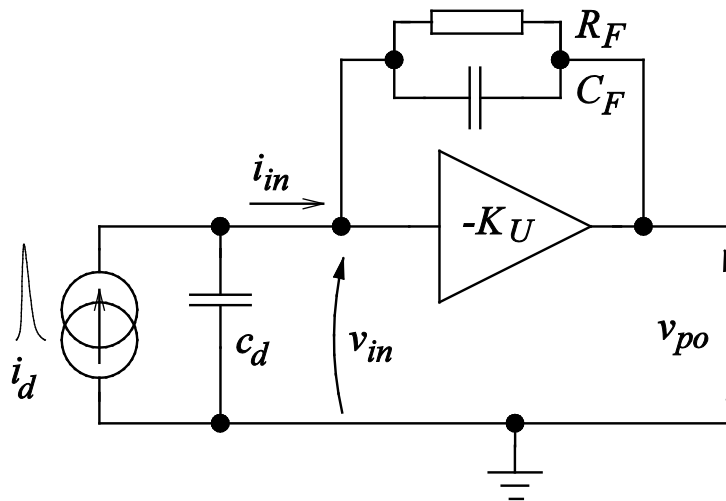

Assuming high  $K_u$  the amplitude response does not depends in first order on  $c_d$ .