
Preamp in charge/transimpedance mode

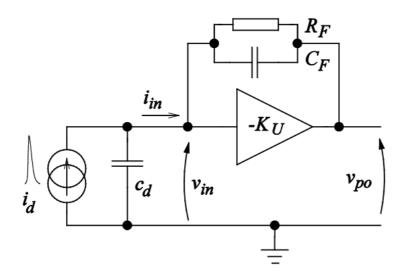

Assuming high Ku the amplitude response does not depends in first order on $c_{\tt d}.$